Circuit Design Practice (3) - Wien-bridge oscillator with JFET AGC

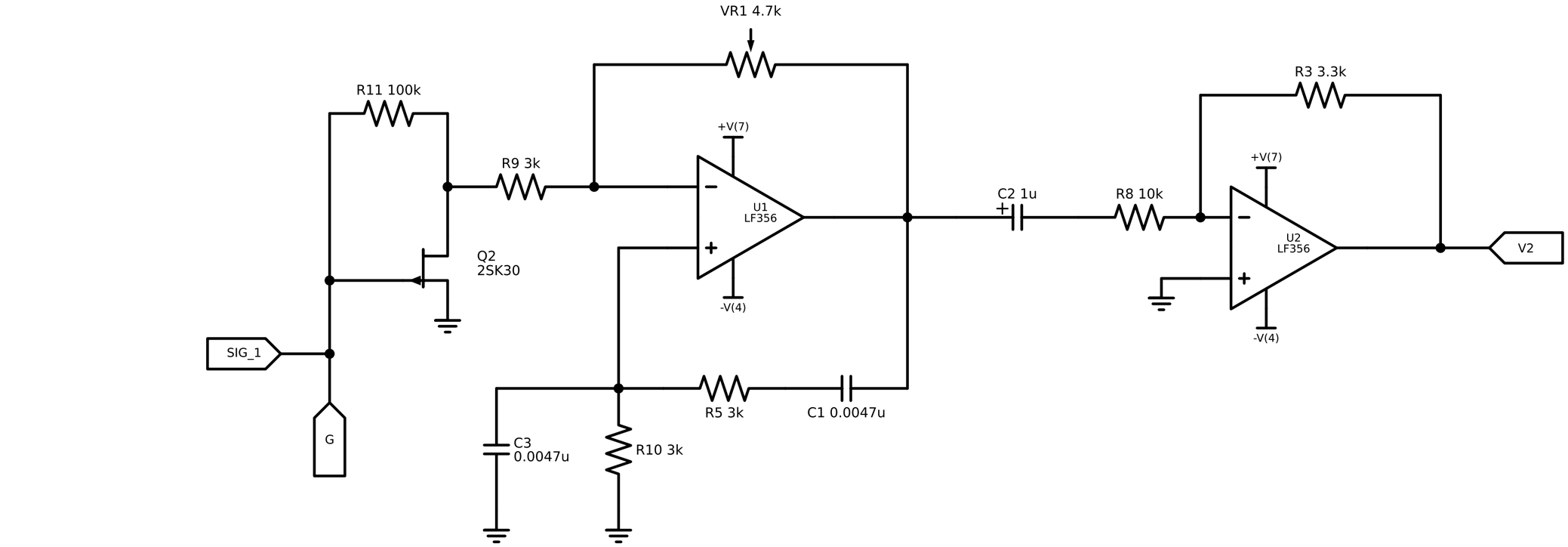

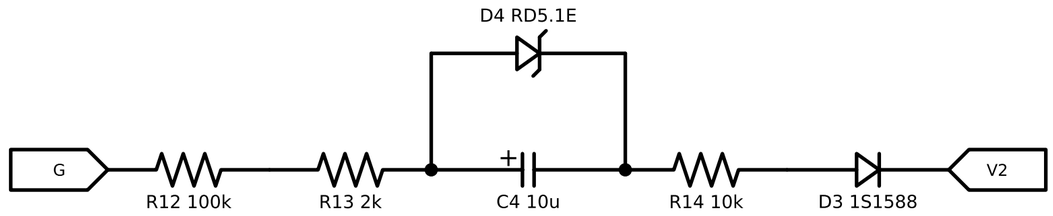

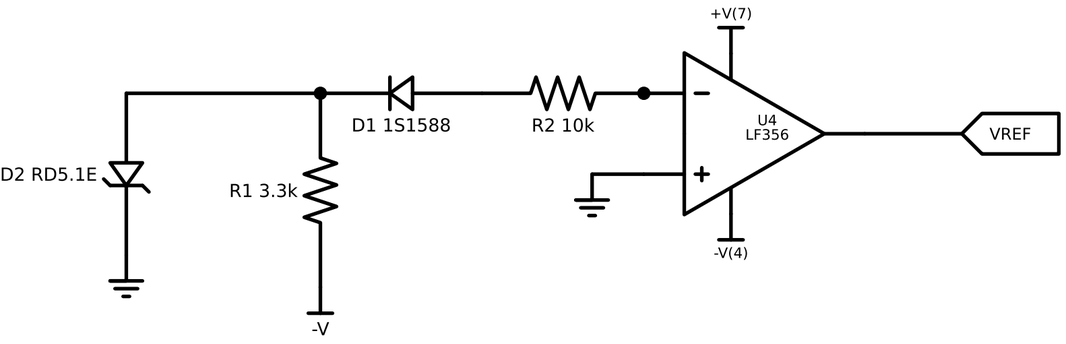

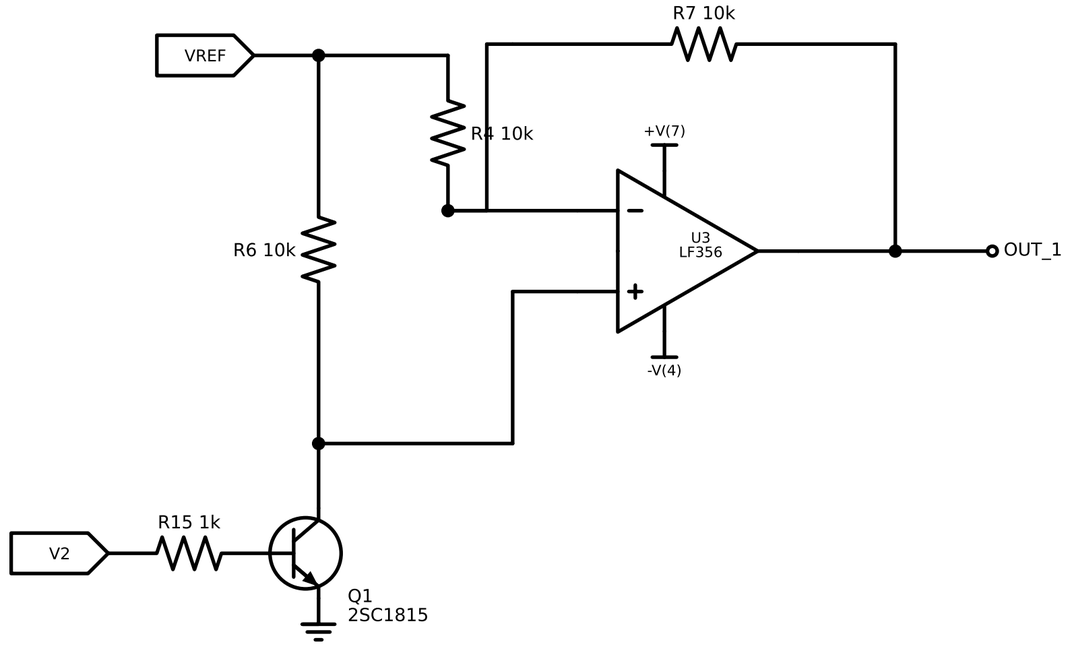

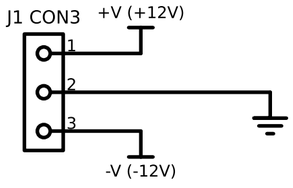

U1~U4 = LF356 : pin7 = +V, pin4 = -V, pin1/5/8 = NC (X)
U4 has no feedback resistor (all R1~R15 are used elsewhere) -> works as comparator